

CS1050 Computer Organization and Digital Design
Lab 5 — Counter with External Input
210113L
Akindu Induwara

Introduction

- In this lab, we have to design a 3-bit counter
- the direction of counting is controlled based on an external input.
- When input button is switched off, counter runs clockwise. When it is switched on, we will count runs anticlockwise


Truth Table

T			B	T+1					
Q2	Q1	Q0		Q2	Q1	Q0+	D2	D1	D0
0	0	0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	1	0	0
0	0	1	0	0	1	1	0	1	1
0	0	1	1	0	0	0	0	0	0
0	1	1	0	1	1	1	1	1	1
0	1	1	1	0	0	1	0	0	1
1	1	1	0	1	1	0	1	1	0
1	1	1	1	0	1	1	0	1	1
1	1	0	0	1	0	0	1	0	0
1	1	0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0	0	0
1	0	0	1	1	1	0	1	1	0

K-Maps


	Q2 Q1				D0 = Q2'.B' +Q1.B
Q0 B	00	01	11	10	
00	1	X	0	0	
01	0	X	1	0	
11	0	X	1	X	
10	1	1	0	X	
	Q2 Q1				D1 = Q0.B' +B.Q2
Q0 B	00	01	11	10	
00	0	X	0	0	
01	0	X	1	1	
11	0	0	1	X	
10	1	1	1	X	
	Q2 Q1				D1 = Q0.B' +B.Q'
Q0 B	00	01	11	10	
00	0	X	1	0	
01	1	X	1	1	
11	0	0	0	X	
10	0	1	1	X	

D_FF - VHDL

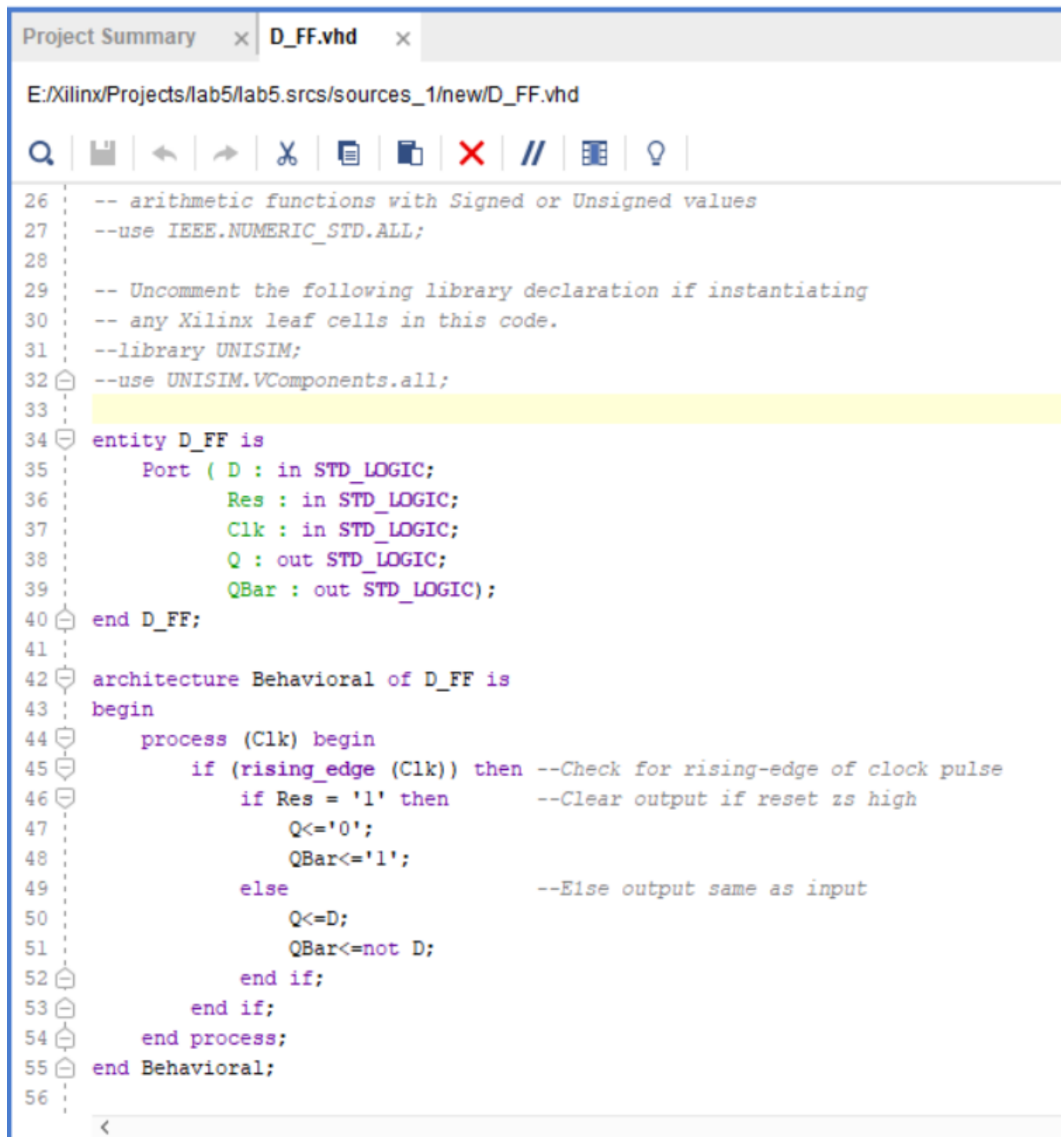


```
26  -- arithmetic functions with Signed or Unsigned values
27  --use IEEE.NUMERIC_STD.ALL;
28
29  -- Uncomment the following library declaration if instantiating
30  -- any Xilinx leaf cells in this code.
31  --library UNISIM;
32  --use UNISIM.VComponents.all;
33
34  entity D_FF is
35      Port ( D : in STD_LOGIC;
36            Res : in STD_LOGIC;
37            Clk : in STD_LOGIC;
38            Q : out STD_LOGIC;
39            QBar : out STD_LOGIC);
40  end D_FF;
41
42  architecture Behavioral of D_FF is
43  begin
44      process (Clk) begin
45          if (rising_edge (Clk)) then --Check for rising-edge of clock pulse
46              if Res = '1' then      --Clear output if reset zs high
47                  Q<='0';
48                  QBar<='1';
49              else                    --Eise output same as input
50                  Q<=D;
51                  QBar<=not D;
52              end if;
53          end if;
54      end process;
55  end Behavioral;
56
```

D_FF_Sim - VHDL

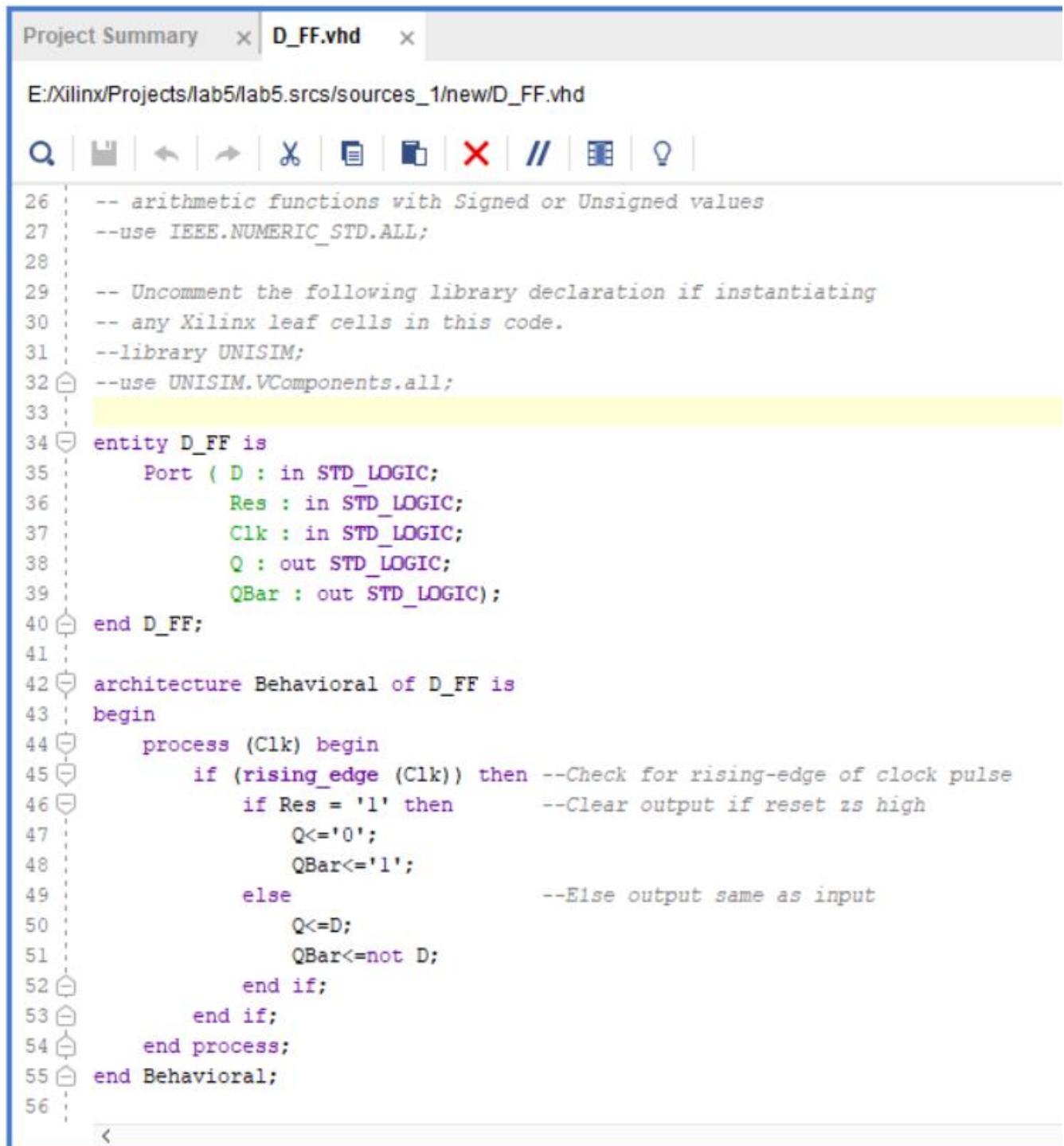


```
26  -- arithmetic functions with Signed or Unsigned values
27  --use IEEE.NUMERIC_STD.ALL;
28
29  -- Uncomment the following library declaration if instantiating
30  -- any Xilinx leaf cells in this code.
31  --library UNISIM;
32  --use UNISIM.VComponents.all;
33
34  entity D_FF is
35      Port ( D : in STD_LOGIC;
36            Res : in STD_LOGIC;
37            Clk : in STD_LOGIC;
38            Q : out STD_LOGIC;
39            QBar : out STD_LOGIC);
40  end D_FF;
41
42  architecture Behavioral of D_FF is
43  begin
44      process (Clk) begin
45          if (rising_edge (Clk)) then --Check for rising-edge of clock pulse
46              if Res = '1' then --Clear output if reset zs high
47                  Q<='0';
48                  QBar<='1';
49              else --Else output same as input
50                  Q<=D;
51                  QBar<=not D;
52              end if;
53          end if;
54      end process;
55  end Behavioral;
```

D_FF_Sim - Time

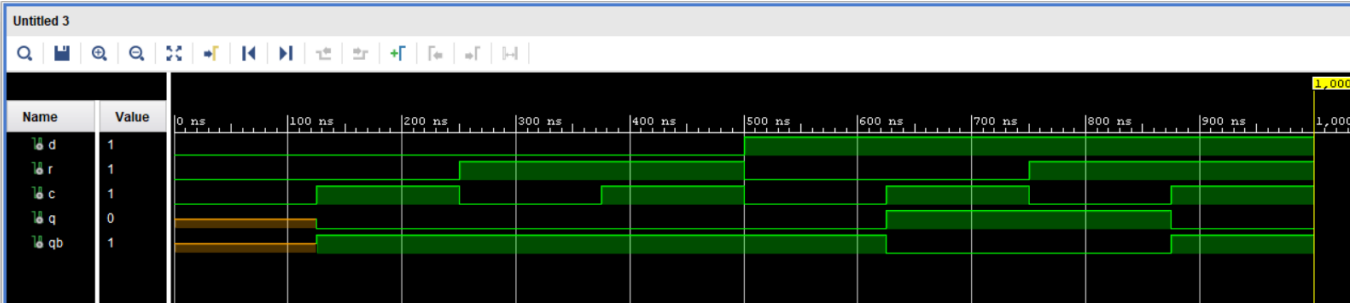

Clk_Slow - VHDL

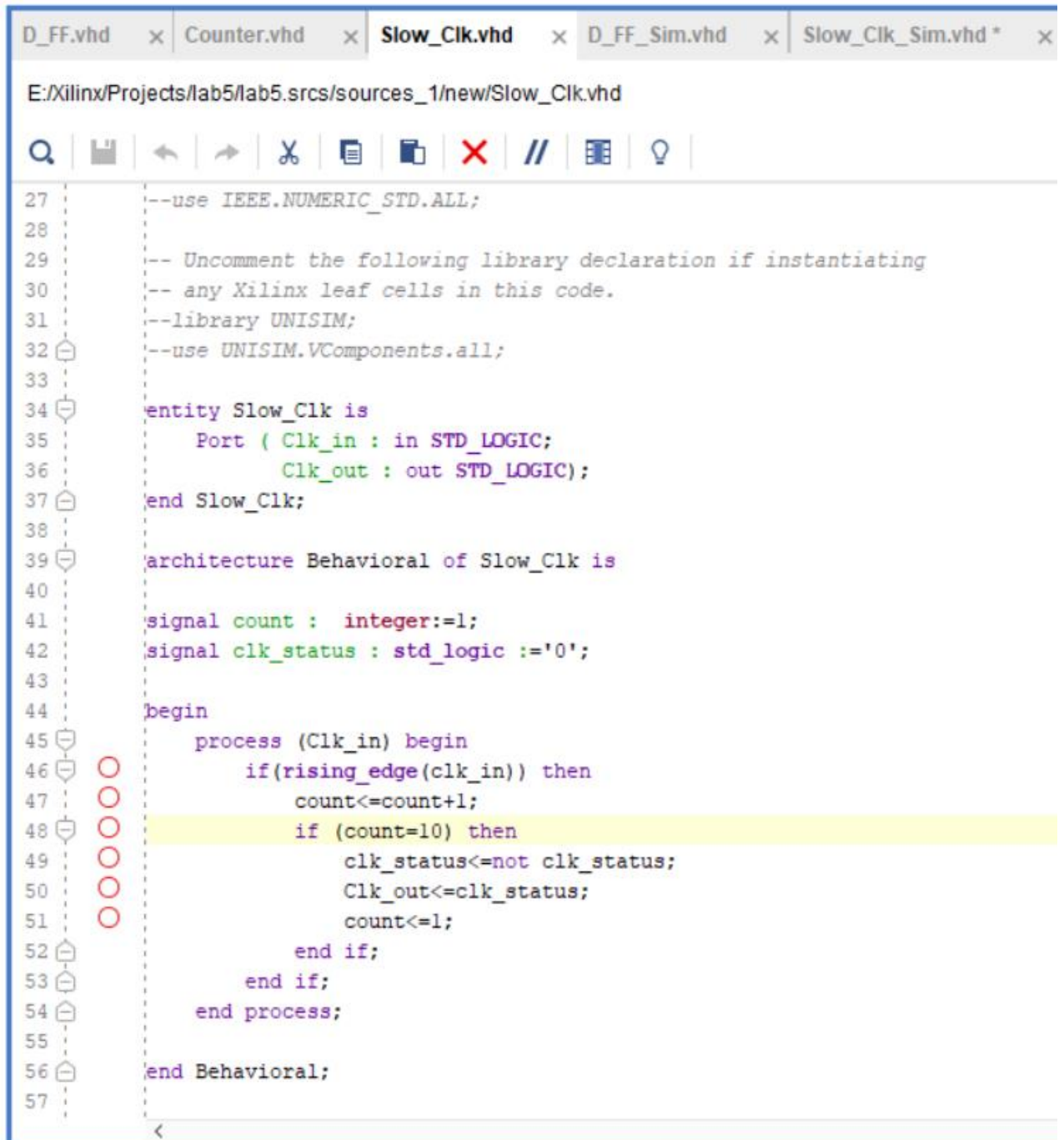


```
27      --use IEEE.NUMERIC_STD.ALL;
28
29      -- Uncomment the following library declaration if instantiating
30      -- any Xilinx leaf cells in this code.
31      --library UNISIM;
32      --use UNISIM.VComponents.all;
33
34      entity Slow_Clk is
35          Port ( Clk_in : in STD_LOGIC;
36                Clk_out : out STD_LOGIC);
37      end Slow_Clk;
38
39      architecture Behavioral of Slow_Clk is
40
41      signal count : integer:=1;
42      signal clk_status : std_logic :='0';
43
44      begin
45          process (Clk_in) begin
46              if(rising_edge(clk_in)) then
47                  count<=count+1;
48                  if (count=10) then
49                      clk_status<=not clk_status;
50                      Clk_out<=clk_status;
51                      count<=1;
52                  end if;
53              end if;
54          end process;
55
56      end Behavioral;
57
```

Clk_Slow_Sim - VHDL

```
D_FF.vhd x Counter.vhd x Slow_Clk.vhd x D_FF_Sim.vhd x Slow_Clk_Sim.vhd * x Counter_Sim.vhd x
E:/Xilinx/Projects/lab5/lab5.srcs/sim_1/new/Slow_Clk_Sim.vhd
[Icons]
24
25 -- Uncomment the following library declaration if using
26 -- arithmetic functions with Signed or Unsigned values
27 --use IEEE.NUMERIC_STD.ALL;
28
29 -- Uncomment the following library declaration if instantiating
30 -- any Xilinx leaf cells in this code.
31 --library UNISIM;
32 --use UNISIM.VComponents.all;
33
34 entity Slow_Clk_Sim is
35 -- Port ( );
36 end Slow_Clk_Sim;
37
38 architecture Behavioral of Slow_Clk_Sim is
39
40 COMPONENT Slow_Clk PORT
41 (Clk_in : in STD_LOGIC;
42 Clk_out : out STD_LOGIC);
43 END COMPONENT;
44 SIGNAL a,b:std_logic;
45
46 begin
47
48 UUT:Slow_Clk PORT MAP(
49 Clk_in =>a,
50 Clk_out=>b
51 );
52
53 process
54 begin
55
56 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
57 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns;
58 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
59 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns;
60 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
61
62 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns;
63 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
64 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns;
65 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
66 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns;
67
68 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
69 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns;
70 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
71 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns;
72 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
73
74 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns;
75 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
76 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns;
77 a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns;
78 a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT FOR 10 ns; a<='1';WAIT FOR 10 ns; a<='0';WAIT;
79 end process;
80
81 end Behavioral;
<
```


Clk_Slow - Time

 

Counter - VHDL

```
Counter.vhd
E:/Xilinx/Projects/lab5/lab5.srscs/sources_1/new/Counter.vhd

20
21
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24
25 -- Uncomment the following library declaration if using
26 -- arithmetic functions with Signed or Unsigned values
27 --use IEEE.NUMERIC_STD.ALL;
28
29 -- Uncomment the following library declaration if instantiating
30 -- any Xilinx leaf cells in this code.
31 --library UNISIM;
32 --use UNISIM.VComponents.all;
33
34 entity Counter is
35     Port ( Dir : in STD_LOGIC;
36           Res : in STD_LOGIC;
37           Clk : in STD_LOGIC;
38           Q : out STD_LOGIC_VECTOR (2 downto 0));
39 end Counter;
40
41 architecture Behavioral of Counter is
42     component D_FF
43     port (
44         D : in STD_LOGIC;
45         Res: in STD_LOGIC;
46         Clk : in STD_LOGIC;
47         Q : out STD_LOGIC;
48         Qbar : out STD_LOGIC);
49 end component;
50
51 component Slow_Clk
52     port (
53         Clk_in : in STD_LOGIC;
54         Clk_out: out STD_LOGIC);
55 end component;
56
57 signal D0, D1, D2 : std_logic;
58 signal Q0, Q1, Q2 : std_logic; -- Internal signals
59 signal Clk_slow : std_logic;
60
61 begin
62     Slow_Clk0 : Slow_Clk
63     port map (
64         Clk_in => Clk,
65         Clk_out => Clk_slow);
66
67     D0 <= ((not Q2) and (not Dir)) or (Q1 and Dir);
68     D1 <= (Q0 and not Dir) or (Q2 and Dir);
69     D2 <= (not Q0 and Dir) or (Q1 and not Dir);
70
71     D_FF0 : D_FF
72     port map (
73         D => D0,
74         Res => Res,
75         Clk => Clk_slow,
76         Q => Q0);
77
78     D_FF1 : D_FF port map (
79         D => D1,
80         Res => Res,
81         Clk => Clk_slow,
82         Q => Q1);
83
84     D_FF2 : D_FF port map (
85         D => D2,
86         Res => Res,
87         Clk => Clk_slow,
88         Q => Q2 );
89
90     Q(0) <= Q0;
91     Q(1) <= Q1;
92     Q(2) <= Q2;
93
94 end Behavioral;
```

Counter_Sim - VHDL

D_FF.vhd
Slow_Clk.vhd
D_FF_Sim.vhd
Slow_Clk_Sim.vhd
Counter_Sim.vhd

E:\Xilinx\Projects\lab5\lab5.srcs\sim_1\new\Counter_Sim.vhd


🔍
📁
⬅️ ➡️
✂️
📄
📁
❌
//
🔧
💡

```

22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24
25 -- Uncomment the following library declaration if using
26 -- arithmetic functions with Signed or Unsigned values
27 --use IEEE.NUMERIC_STD.ALL;
28
29 -- Uncomment the following library declaration if instantiating
30 -- any Xilinx leaf cells in this code.
31 --library UNISIM;
32 --use UNISIM.VComponents.all;
33
34 entity Counter_Sim is
35 -- Port ( );
36 end Counter_Sim;
37
38 architecture Behavioral of Counter_Sim is
39
40 COMPONENT Counter_PORT
41 ( Dir,Res,Clk : in STD_LOGIC;
42 Q : out STD_LOGIC_VECTOR (2 downto 0));
43 END COMPONENT;
44
45 SIGNAL Dir,Res,Clk : std_logic;
46 SIGNAL Q : std_logic_vector(2 downto 0);
47
48 begin
49 UUT: Counter_PORT MAP(
50 Dir => Dir,
51 Res => Res,
52 Clk => Clk,
53 Q=>Q
54 );
55
56 process
57 begin
58 Dir <= '0';
59 Res <= '1';
60 for i in 1 to 20 loop
61 Clk <= '0';
62 WAIT FOR 2 ns;
63 Clk <= '1';
64 WAIT FOR 2 ns;
65 end loop;
66 WAIT FOR 50 ns;
67 Res <= '0';
68 for i in 1 to 200 loop
69 Clk <= '0';
70 WAIT FOR 2 ns;
71 Clk <= '1';
72 WAIT FOR 2 ns;
73 end loop;
74 Dir <= '1';
75 WAIT FOR 50 ns;
76 for i in 1 to 200 loop
77 Clk <= '0';
78 WAIT FOR 2 ns;
79 Clk <= '1';
80 WAIT FOR 2 ns;
81 end loop;
82 WAIT;
83
84 end process;
85 end Behavioral;

```

Counter - Time

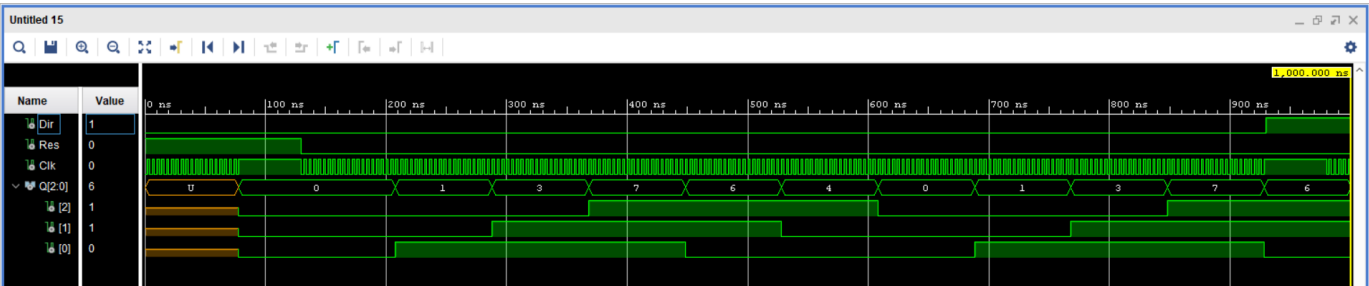

Conclusion

- The 3-bit counter is built using relatively simple component such as D flip flops and combinational logic circuits. This shows hierarchical design.
- The inbuilt clock of basys board is used is to give the clock signal for the logic unit.
- In VHDL we can define how a circuit should behave more abstractly. This is known as VHDL Behavioral Modelling. It allows us to use high-level programming constructs such as variables, conditions, procedures and loops in our code.